

# CSE 331 Computer Organizations Homework 3

Fatih Kaan Salgır - 171044009

## 1 Datapath


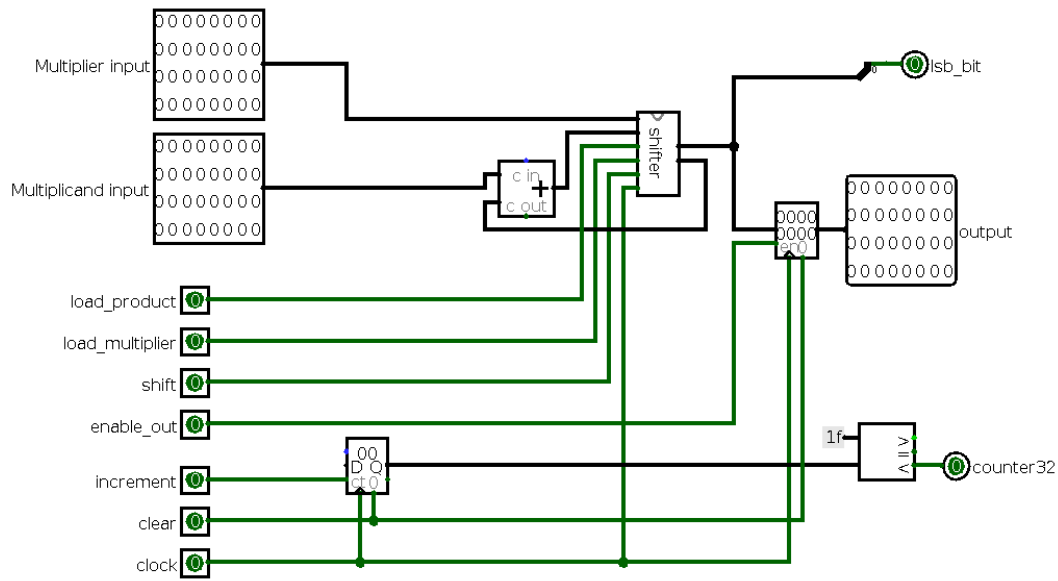


Figure 1: Datapath

- To avoid glitches on the output, I put a register before the output and enabled on the last state. (**enable\_out**)
- Counter and comparator are 6 bits (They could be 5 bits, but I preferred this way to simplify state diagram).
- **clear** will clear both counter and contents of the output register after.
- **increment** will increment the counter, so that we can check if we reach 32. In this case machine will go to last state.

## 1.1 Shifter

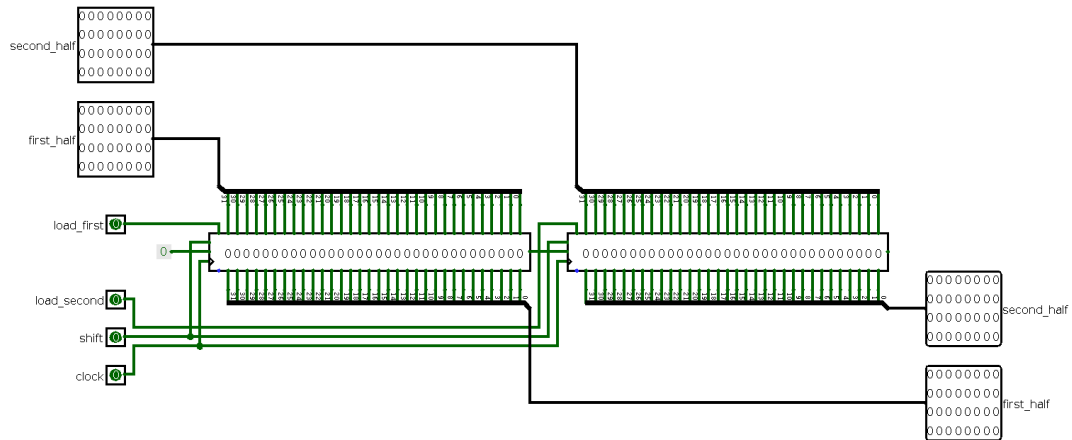

- I have used 2 32-bit shift register by connecting first shifter's output bit to second shifter's input bit.
- Since our fsm will be responsible calculating unsigned numbers, first shifter's input bit should be 0.
- **load\_first** and **load\_second** signals will load the values to registers.
- **shift** signal will shift both registers to right.

## 2 State Diagram

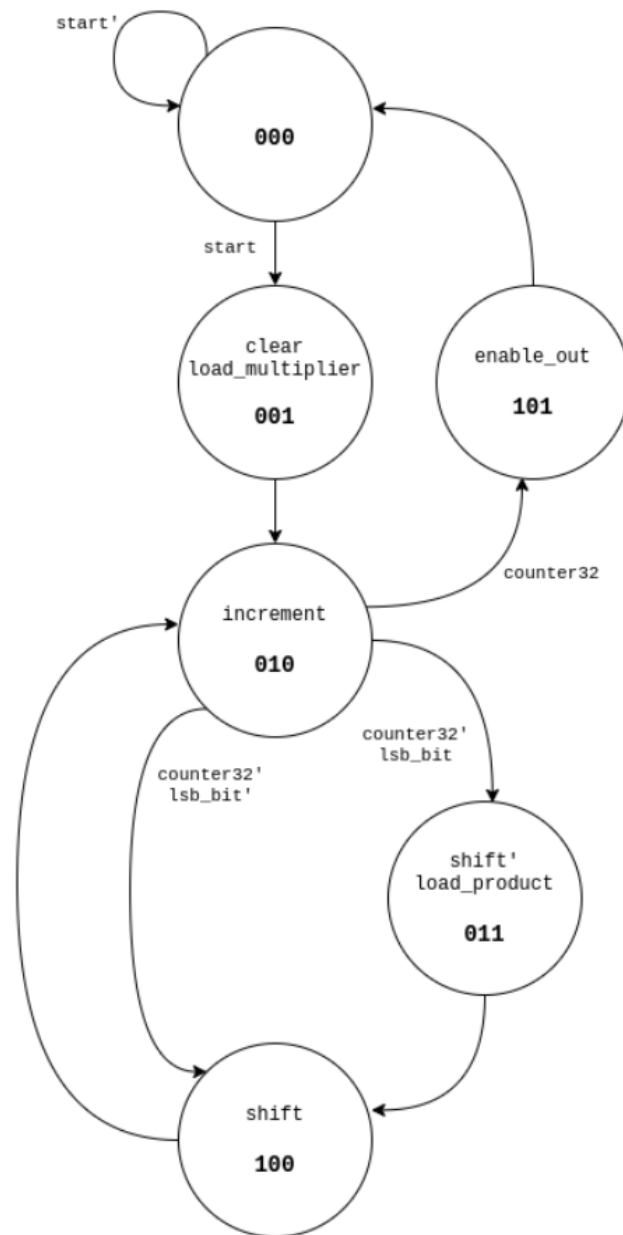


Figure 2: FSM

### 3 Designing Control Unit

#### 3.1 Truth Table

Table 1: Next state according to present state and inputs

s2	s1	s0	start	counter32	lsb_bit	n2	n1	n0
0	0	0	0	X	X	0	0	0
0	0	0	1	X	X	0	0	1
0	0	1	X	X	X	0	1	0
0	1	0	X	1	X	1	0	1
0	1	0	X	0	0	1	0	0
0	1	0	X	0	1	0	1	1
0	1	1	X	X	X	1	0	0
1	0	0	X	X	X	0	1	0
1	0	1	X	X	X	0	0	0

$$n2 = s2' s1 s0' counter32 + s2' s1 s0' counter32' lsb\_bit' + s2' s1 s0$$

$$n2 = s2' s1 s0' ( counter32 + counter32' lsb\_bit' ) + s2' s1 s0$$

$$n2 = s2' s1 s0' ( counter32 + lsb\_bit' ) + s2' s1 s0$$

$$n2 = s2' s1 ( s0' ( counter32 + lsb\_bit' ) + s0 )$$

$$n2 = s2' s1 ( counter32 + lsb\_bit' + s0 )$$

$$n1 = s2' s1' s0 + s2' s1 s0' counter32' lsb\_bit + s2 s1' s0'$$

$$n1 = s1' ( s2' s0 + s2 s0' ) + s2' s1 s0' counter32' lsb\_bit$$

$$n1 = s1' ( s2 \text{ XOR } s0 ) + s2' s1 s0' counter32' lsb\_bit$$

$$n0 = s2' s1' s0' start + s2' s1 s0' counter32 + s2' s1 s0' counter32' lsb\_bit$$

$$n0 = s2' s1' s0' start + s2' s1 s0' ( counter32 + counter32' lsb\_bit )$$

$$n0 = s2' s1' s0' start + s2' s1 s0' ( counter32 + lsb\_bit )$$

Table 2: Inputs according to states

s2	s1	s0	load_product	load_multiplier	shift	enable_out	increment	clear
0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	1
0	1	0	0	0	0	0	1	0
0	1	1	1	0	0	0	0	0
1	0	0	0	0	1	0	0	0
1	0	1	0	0	0	1	0	0

load\_product = s2' s1 s0

load\_multiplier = s2' s1' s0

shift = s2 s1' s0'

enable\_out = s2 s1' s0

increment = s2' s1 s0'

clear = s2' s1' s0

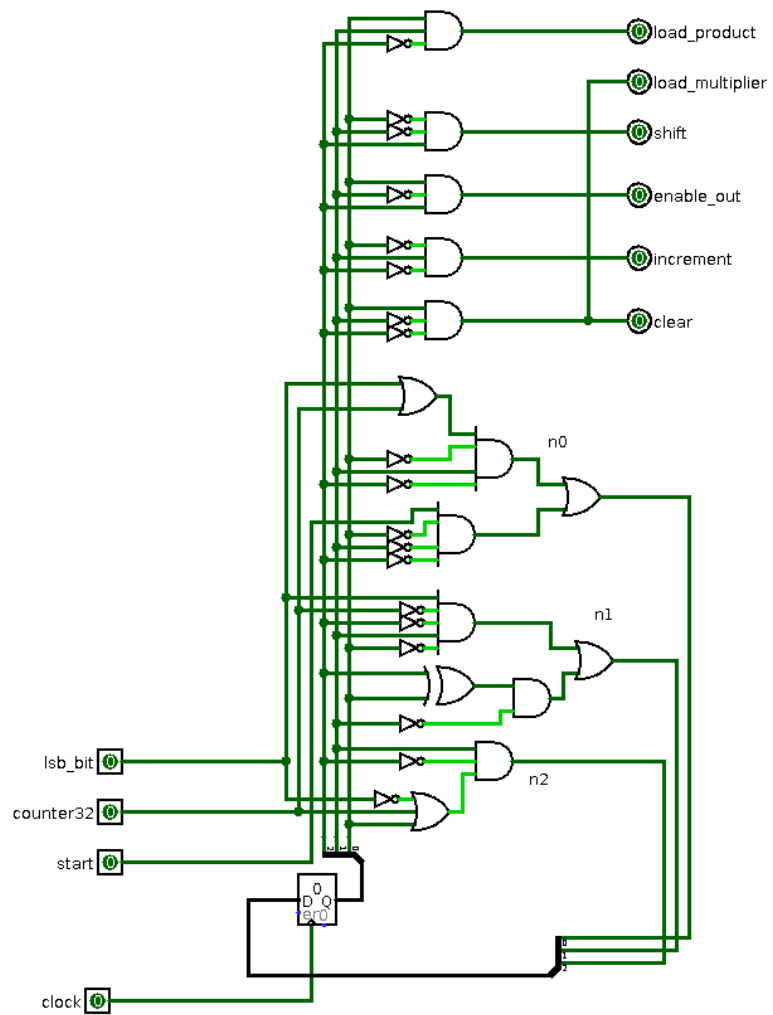


Figure 3: Control Unit

## 4 Connecting Datapath and Control Unit & Tests

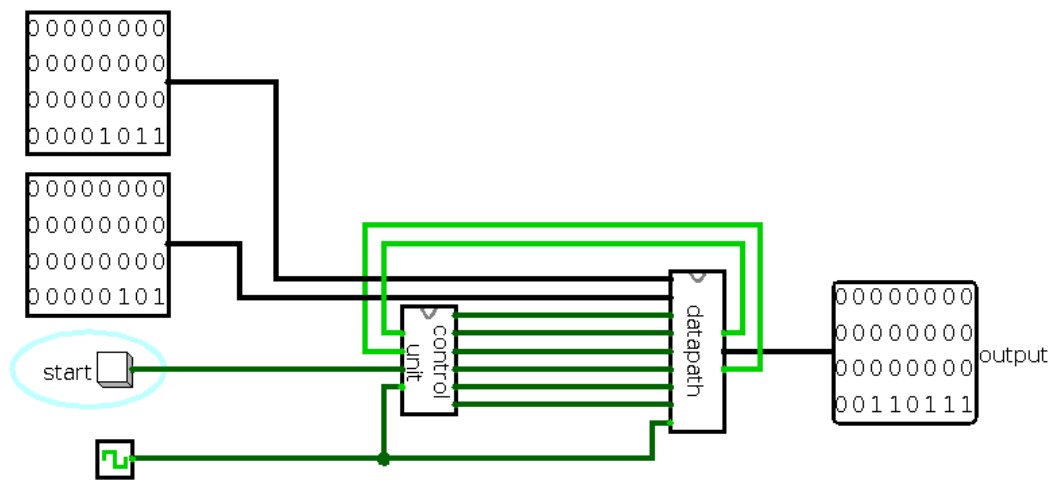


Figure 4:  $11 \times 5 = 55$

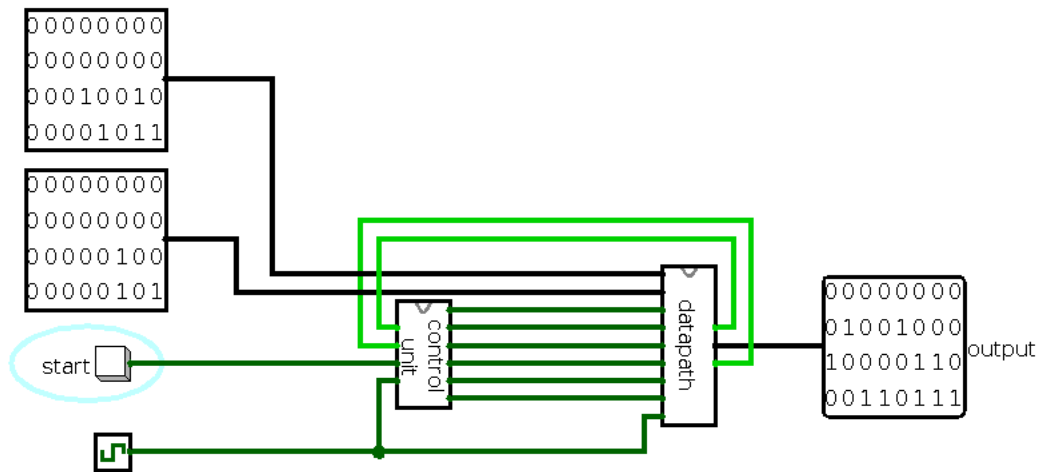


Figure 5:  $4619 \times 1029 = 4752951$

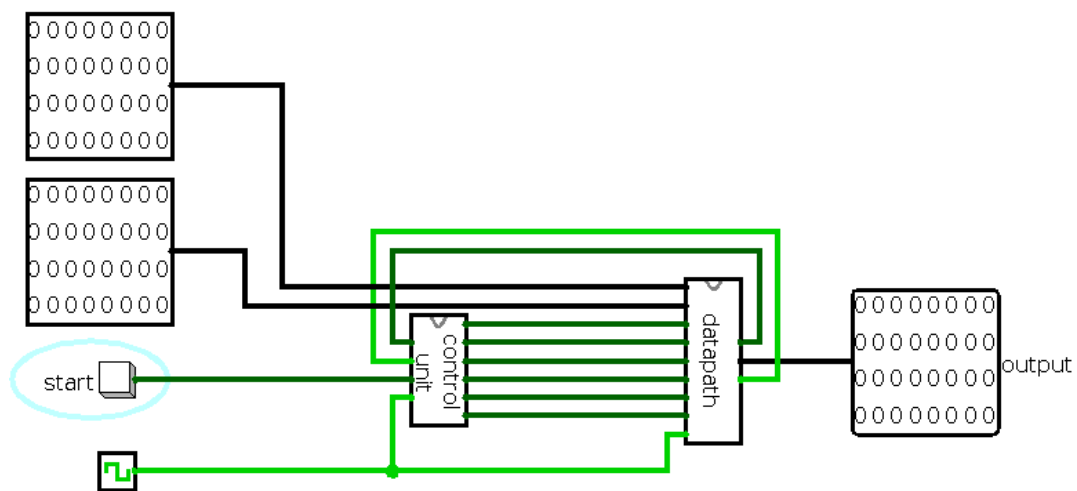


Figure 6:  $0 \times 0 = 0$

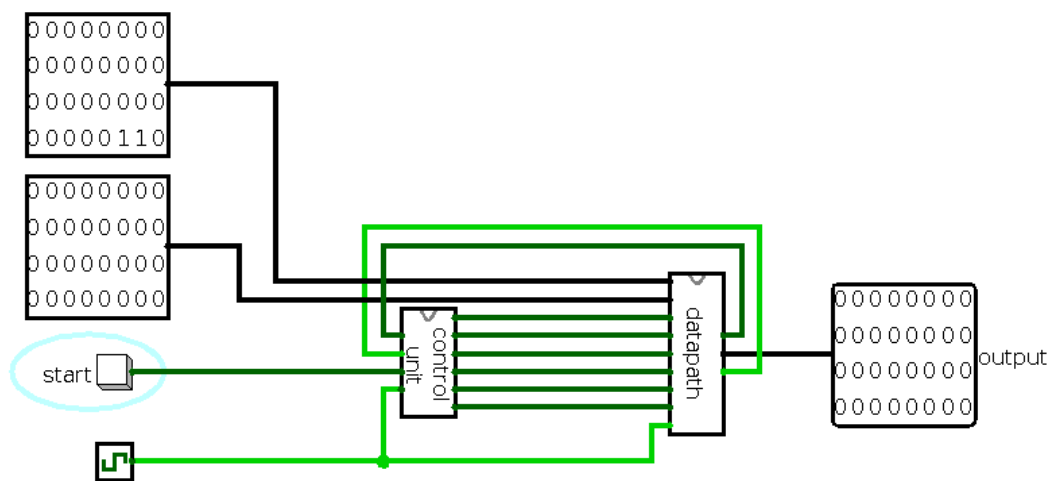


Figure 7:  $6 \times 0 = 0$



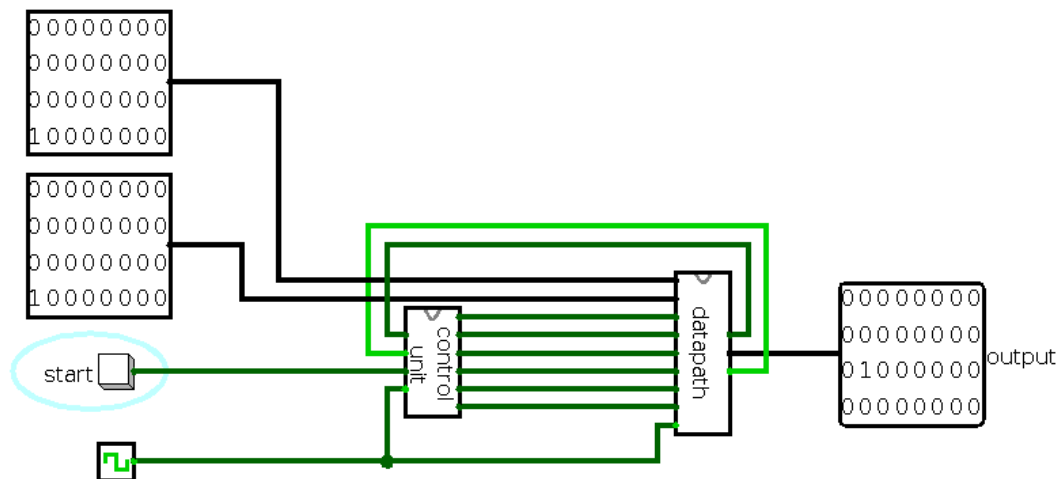


Figure 8:  $128 \times 128 = 16384$

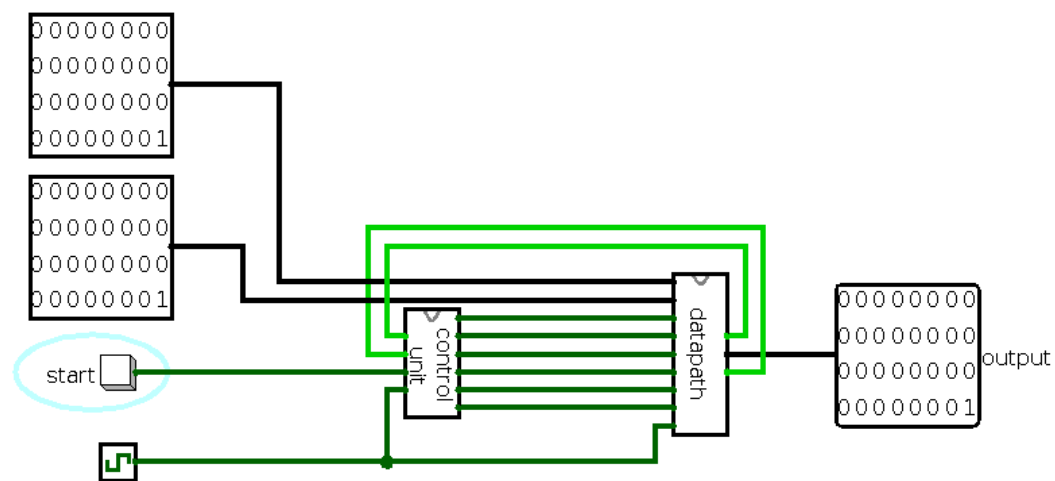


Figure 9:  $1 \times 1 = 1$